

# Section 7.2: Logic Networks


April 14, 2008

## Abstract

We examine the relationship between the abstract structure of a Boolean algebra and the practical problem of creating logic networks for solving problems. There is a fundamental equivalence between Truth Functions, Boolean Expressions, and Logic Networks which allows us to pass from one to the other.

## 1 An Example Application, and Fundamental Parallels

Example: Two light switches, one light!

 

The problem is as follows: A light at the bottom of some stairs is controlled by two light switches, one at each end of the stairs. The two switches should be able to control the light independently. How do we wire the light?

- A Truth Function

$s_1$	$s_2$	$L$
on	on	on
on	off	off
off	on	off
off	off	on

$L(s_1, s_2)$

$s_1$	$s_2$	$L$
1	1	1
1	0	0
0	1	0
0	0	1


$$L = (s_1 \wedge s_2) \vee (s_1' \wedge s_2')$$

- A Boolean Expression


$$L = s_1 \cdot s_2 + s_1' \cdot s_2'$$

$$= s_1 \cdot s_2 + (s_1 + s_2)'$$

(builds a slightly tidier Logic network)

 


# (Minimization)

 


## • A Logic Network (Basic Mechanics and Conventions)

– Input or output lines are not tied together except by passing through gates:

- \* OR gate
- \* AND gate

 

\* NOT gate

 

- Lines can be split to serve as input to more than one device.
- There are not loops with output of a gate serving as input to the same gate (feedback).
- There are no delay elements.

## 2 Applications

### 2.1 Converting Truth Tables to Boolean Expressions (Canonical Sum-of-Products Form)

Example: Practice 11, p. 485/558

$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
1	1	1	1
1	1	0	0
1	0	1	1
1	0	0	1
0	1	1	0
0	1	0	0
0	0	1	1
0	0	0	1

$$f(x_1, x_2, x_3) =$$

$$x_1 x_3 \left\{ \begin{array}{l} x_1 x_2 x_3 + \\ x_1 x_2' x_3 + \\ x_1 x_2' x_3' + \end{array} \right\} x_1 x_2'$$

$$x_1' x_2' \left\{ \begin{array}{l} x_1' x_2' x_3 + \\ x_1' x_2' x_3' \end{array} \right.$$

$$x_1 x_2 x_3 + x_1 x_2' x_3 = x_1 x_3 (x_2 + x_2') = x_1 x_3 \cdot 1 = x_1 x_3$$

$$f(x_1, x_2, x_3) = x_1 x_3 + \underline{x_1 x_2' + x_1' x_2'}$$

$$= x_1 x_3 + x_2'$$

Example: Exercise 10/11, p. 495/568

$$f(x_1, x_2, x_3) = \left. \begin{array}{l} x_1 x_2' x_3 + \\ x_1 x_2' x_3' + \\ x_1' x_2 x_3' \end{array} \right\} x_1 x_2'$$

$$x_3' (x_1 x_2' + x_1' x_2)$$

$$f(x_1, x_2, x_3) = x_1 x_2' + x_1' x_2 x_3'$$

(Can we do better?)

### 2.2 Converting Boolean Expressions to Logic Networks


Example: Exercise 1b, p. 493/566

(Simplify first!)

$$(x_1 + x_2)' + x_1' x_3$$


$$= x_1' \cdot x_2' + x_1' x_3$$

$$= x_1' \cdot (x_2' + x_3)$$

 

## 2.3 Converting Logic Networks to Truth Functions or Boolean Expressions

Example: Exercise 2, p. 493/567

 

$$(x_1 \cdot x_2) + x_2' = f(x_1, x_2)$$

$x_1$	$x_2$	$f(x_1, x_2)$
1	1	1
1	0	1
0	1	0
0	0	1

$$f(x_1, x_2) = (x_1' \cdot x_2)'$$

$$= x_1 + x_2'$$

$$= x_1 \cdot x_2 + x_2'$$

## 2.4 Simplifying Canonical Form


We can use properties of Boolean algebra to simplify the canonical form, creating a much simpler logic network as a result.

Example: Practice 11, p. 485/558

*(Already did this above)*

## 2.5 Adding Binary numbers

Half-Adders and Full-Adders

 

$x_1$	$x_2$	$s$	$c$
1	1	0	1
1	0	1	0
0	1	1	0
0	0	0	0

Half-Adder: Adds two binary digits.

written:  $s = x_1'x_2 + x_1x_2'$

Carried:  $c = x_1x_2$

Note, however, that the half-adder doesn't implement  $s$  in this way: instead,

$$s = (x_1 + x_2) \cdot (x_1x_2)' = (x_1 + x_2)(x_1' + x_2')$$

$$= \cancel{x_1x_1'} + x_1x_2' + x_2x_1' + \cancel{x_2x_2'} \quad \checkmark$$

Questions:

1 How?

2 Why? *Re-use the carry digit calculation!*

Full-Adder: Adds two digits plus the carry digit (made up of two half-adders, essentially!).

- Give  $c_{i-1}, x_i, y_i$
- Simply use a half-adder to add the carry digit  $c_{i-1}$  to the sum digit  $s$  of a half-adder of  $x_i, y_i$ , to get  $s_i$ .
- To get the carry digit  $c_i$ , compare carry digits of both half-adders, to see if either gives a 1 (in which case  $c_i = 1$ ).

Example: Practice 12, p. 490/563

