


Homework § 8.2, #14, 30, 33

#14: you just read off the table
(those rows featuring 1 for $f(x_1, x_2, x_3)$):

$$f(x_1, x_2, x_3) = x_1 x_2 x_3' + x_1 x_2' x_3 + x_1' x_2 x_3 + x_1' x_2' x_3'$$
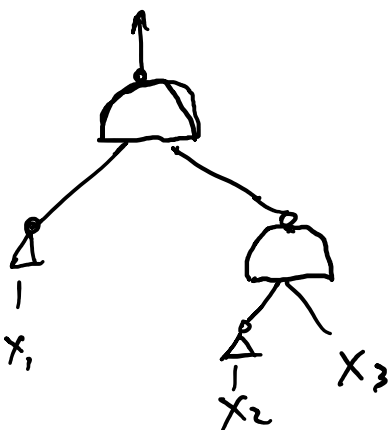
#30: Were to replace a network with
NAND gates & invertors with an
equivalent logic network using one
AND, one OR, & an invertor (simplifying
the logic network by one unit).

Just reading off the logic network
(+ perhaps thinking of it as a tree,
& an in-order traversal):




$$x_1' \text{ NAND } (x_2' \text{ NAND } x_3)$$

or $(x_1' \wedge (x_2' \wedge x_3))'$

or $x_1 \vee ((x_2' \wedge x_3)')$ (\Rightarrow) $x_1 \vee (x_2' \wedge x_3)$

Here it is: one or, and, + in vector:

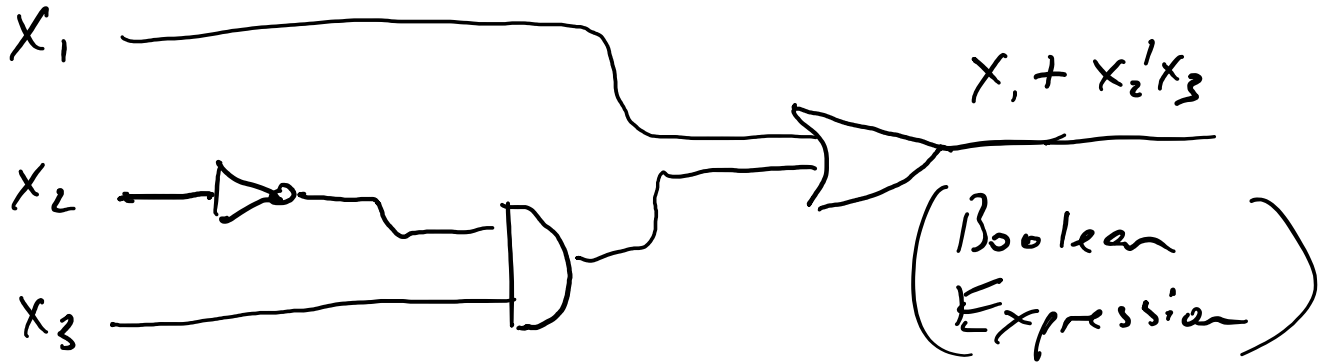

#33 An interesting example, similar to my light fixture problem:

$$x_1 = \begin{cases} 1 & \text{when } T < 67^\circ\text{F} \\ 0 & \text{otherwise} \end{cases}$$

$$x_2 = \begin{cases} 1 & \text{when } t < 7\text{am} \vee t > 6\text{pm} \\ 0 & \text{otherwise} \end{cases}$$

We want the heat to come on when

$$T < 67 \wedge 7\text{am} \leq t \leq 6\text{pm}$$

That is, $x_1 \wedge (x_2)'$

In terms of truth tables
(functions)

x_1	x_2	$f(x_1, x_2)$
1	1	0
1	0	1
0	1	0
0	0	0

$$x_1 \cdot x_2' = f(x_1, x_2)$$

