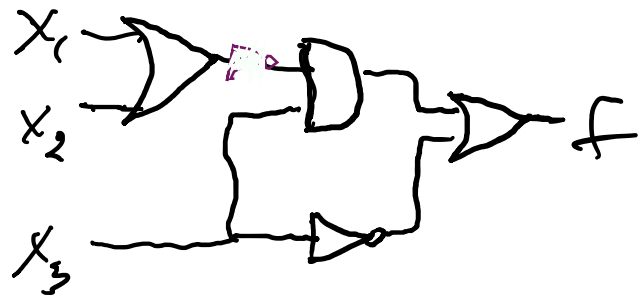


Ex 8.2 # 4, 14, 29

4] $(x_1 + x_2)' x_3 + x_3' = f(x_1, x_2, x_3)$

Write a truth function
a logic network

x_1	x_2	x_3	$f(x_1, x_2, x_3)$
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	1
0	0	0	1



$$\#14 \quad f(x_1, x_2, x_3) = x_1 x_2 x_3' +$$

$$x_1 x_2' x_3 +$$

$$x_1' x_2 x_3 +$$

$$x_1' x_2' x_3'$$

$$\#29 \quad x_2' x_1 + x_2' x_1 + x_3' = f(x_1, x_2, x_3)$$

x_1	x_2	$(x_1 \bullet x_2)'$
1	1	0
1	0	1
0	1	1
0	0	1

As seen on page
(65), we can
replace and ors
with the units
in figure 8.17.


I'm going to simplify a little before
step 2.:

$$x_3' x_1 + x_3' + x_2' x_1$$


$$= x_3' (x_1 + 1) + x_2' x_1$$

$$= x_3' + x_2' x_1$$



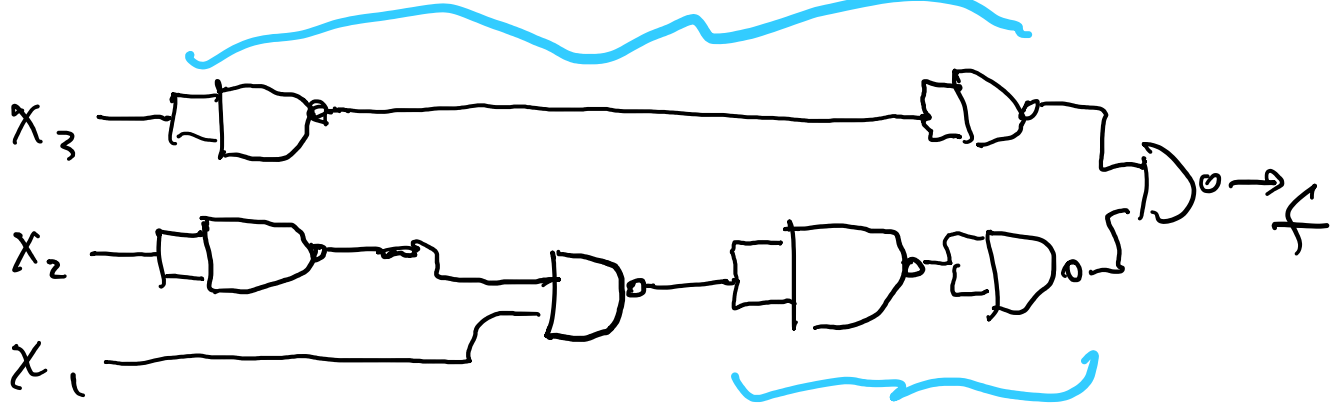

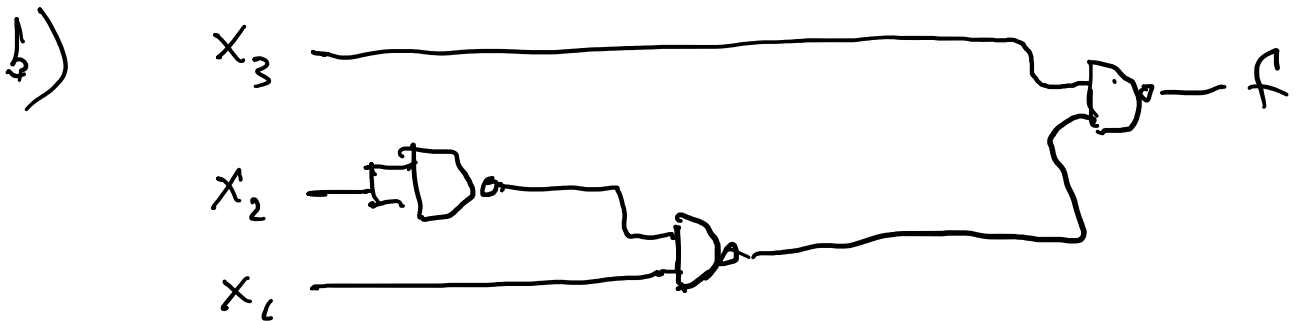When we see two negations in a row we can simplify!



So this did the simplification for me!

$$f(x_1, x_2, x_3) = (x_3 \cdot (x_2' \cdot x_1)')'$$

$$= x_3' + x_2' \cdot x_1$$

Note: This is slightly simpler

than the one given in the back
of the book :

$$f(x_1, x_2, x_3) = x_1 (x_3' + x_2') + x_3'$$

this one
contributes
nothing, since

$$= \left((x_3 \cdot x_2)' \cdot x_1 \right) \cdot x_3'$$

$$= \left(x_1 \cdot (x_2 \cdot x_3)' \right) \cdot x_3'$$

